



3

3.1

3.2

3.3

3.4

3.5



3

1.

2.

3.

4.

3




1.

2.

3.1



3.1.1

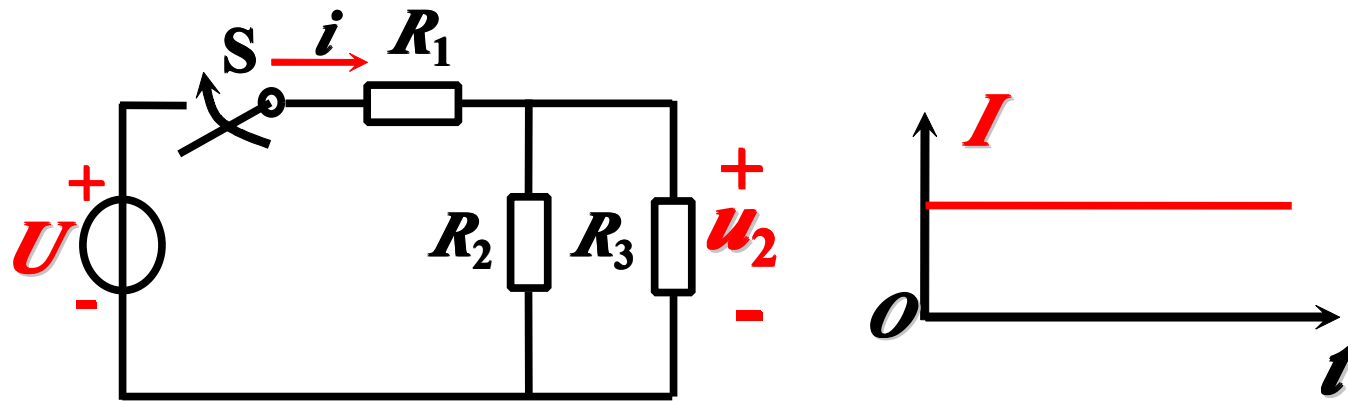


(a)

(a) S $i = 0$ $u_{R1} = u_{R2} = u_{R3} = 0$

S i u

(R)

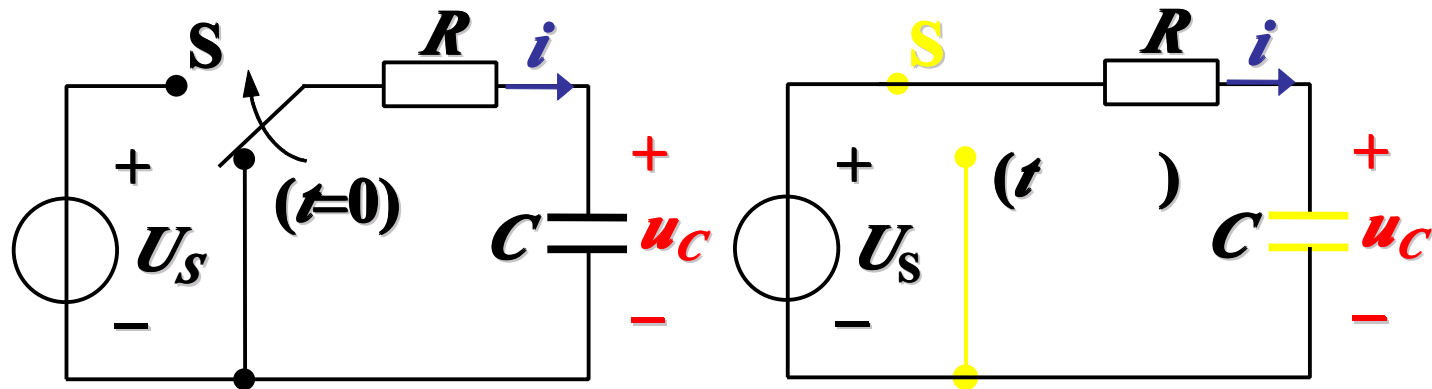



S

$$i = 0, u_C = 0$$

S

$$i = 0, u_C = U_s$$

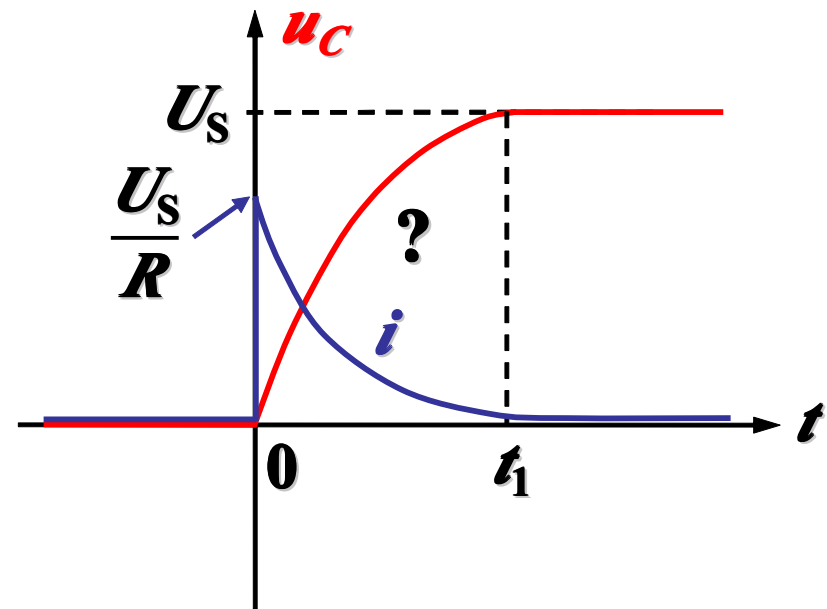

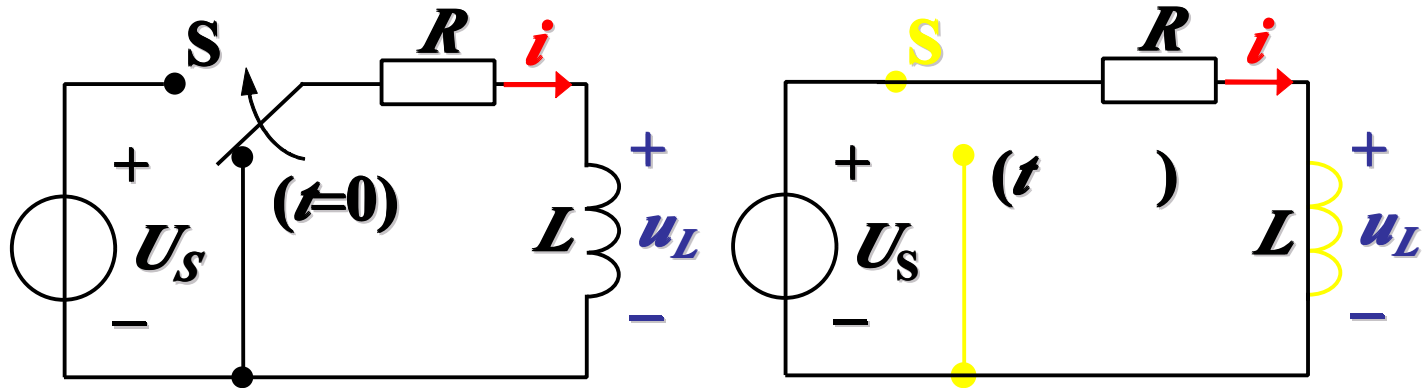


S

$$i = 0, u_L = 0$$

S

$$u_L = 0, i = \frac{U_s}{R}$$

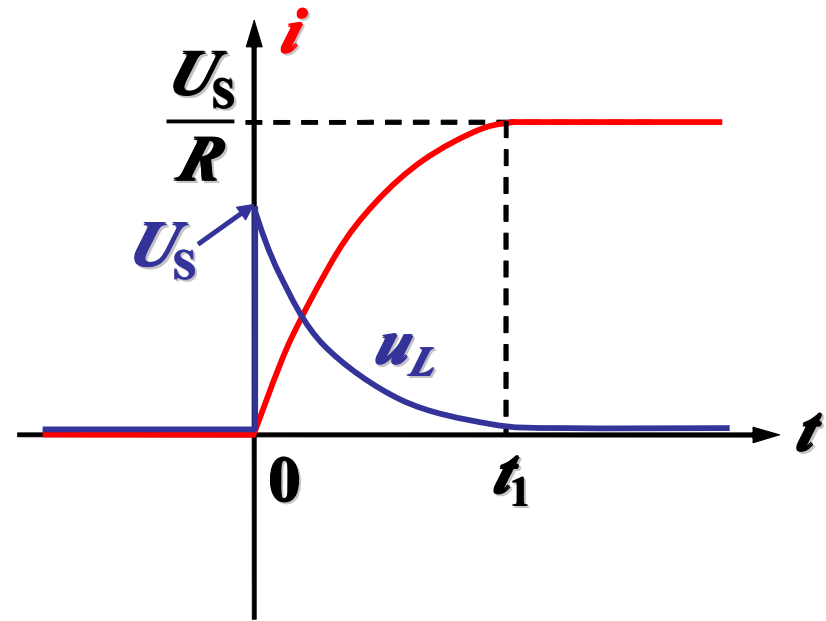



⋮

C


$$W_C = \frac{1}{2} C u_C^2$$

∴ ***u_C***


L

$$W_L = \frac{1}{2} L i_L^2$$

∴ ***i_L***

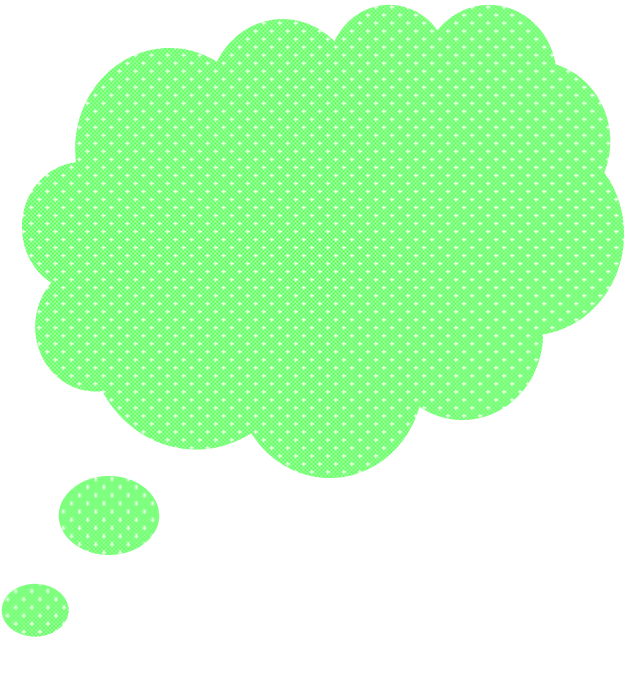

3.1.2

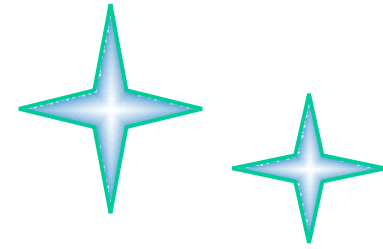

$t=0$ —

()

$t=0_-$ —

$t=0_+$ —

$t=\infty$ —

$$i_L(0_+) = i_L(0_-)$$

$$u_C(0_+) = u_C(0_-)$$

u_C i_L

3.1.3



$$u \quad i \quad t=0_+$$

$$(1) \quad u_C(0_+) \quad i_L(0_+)$$

$$1) \quad t=0_- \quad u_C(0_-) \quad i_L(0_-)$$

$$2) \quad u_C(0_+) \quad i_L(0_+)$$

(2)


$$1) \quad t=0_+$$

$$2) \quad t=0_+ \quad u_C = u_C(0_+)$$

$$t=0_+ \quad i_L = i_L(0_+)$$



1

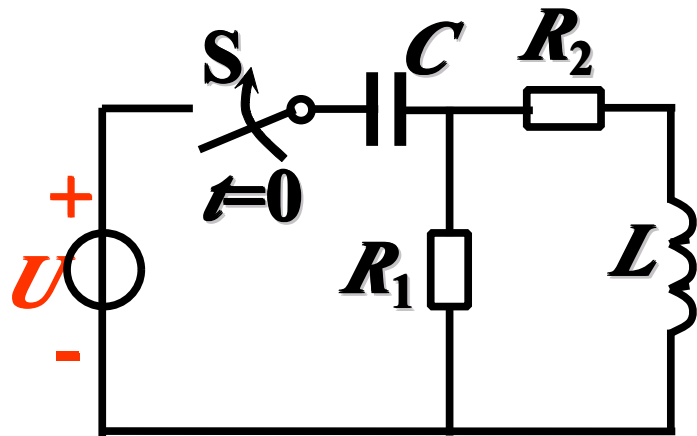

(a)

(1)


$$u_C(0_-), i_L(0_-)$$

$$u_C(0_-) = 0, i_L(0_-) = 0$$


$$u_C(0_+) = u_C(0_-) = 0$$

$$i_L(0_+) = i_L(0_-) = 0$$

1:

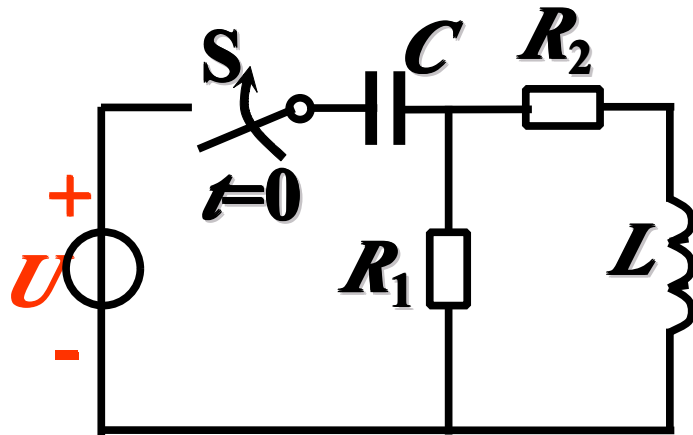

(a)

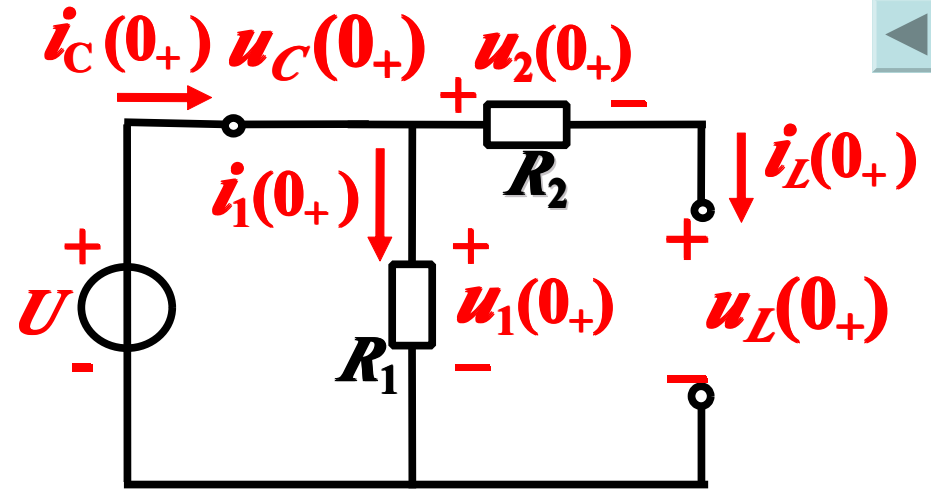

(b) $t = 0+$

(2) $t = 0_+$

$$u_C(0_-) = 0,$$

$$i_L(0_-) = 0,$$

$$i_C(0_+) = i_1(0_+) = \frac{U}{R}$$

$$u_L(0_+) = u_1(0_+) = U$$


$$(i_C(0_-) = 0)$$

$$(u_L(0_-) = 0)$$

i_C u_L

$$u_2(0_+) = 0$$


2

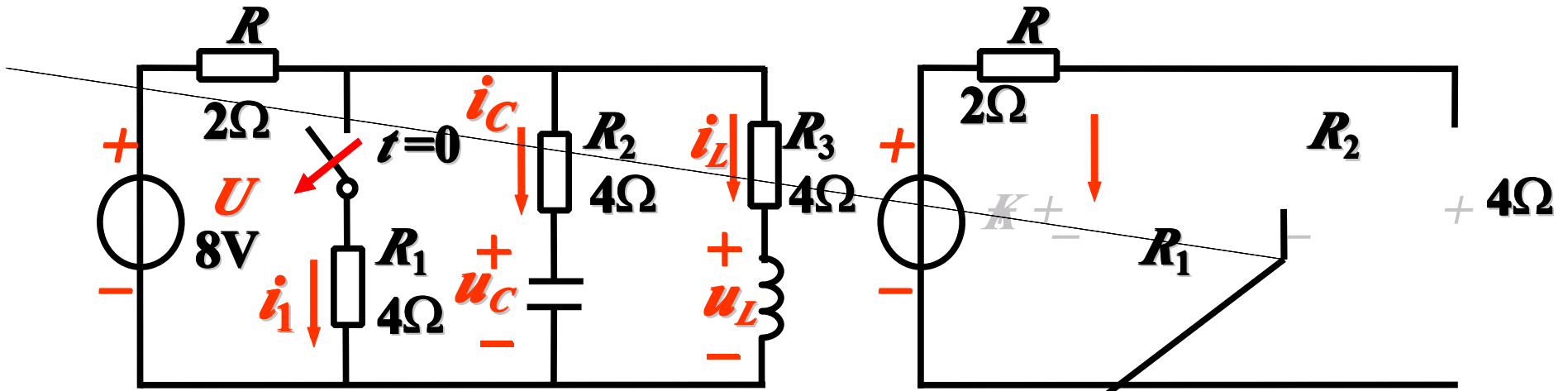

(1) $t = 0_-$ $u_C(0_-)$ $i_L(0_-)$

$$i_L(0_-) = \frac{R_1}{R_1 + R_3} \times \frac{U}{R + \frac{R_1 R_3}{R_1 + R_3}} = \frac{4}{4 + 4} \times \frac{U}{2 + \frac{4 \times 4}{4 + 4}} = 1 \text{ A}$$

2

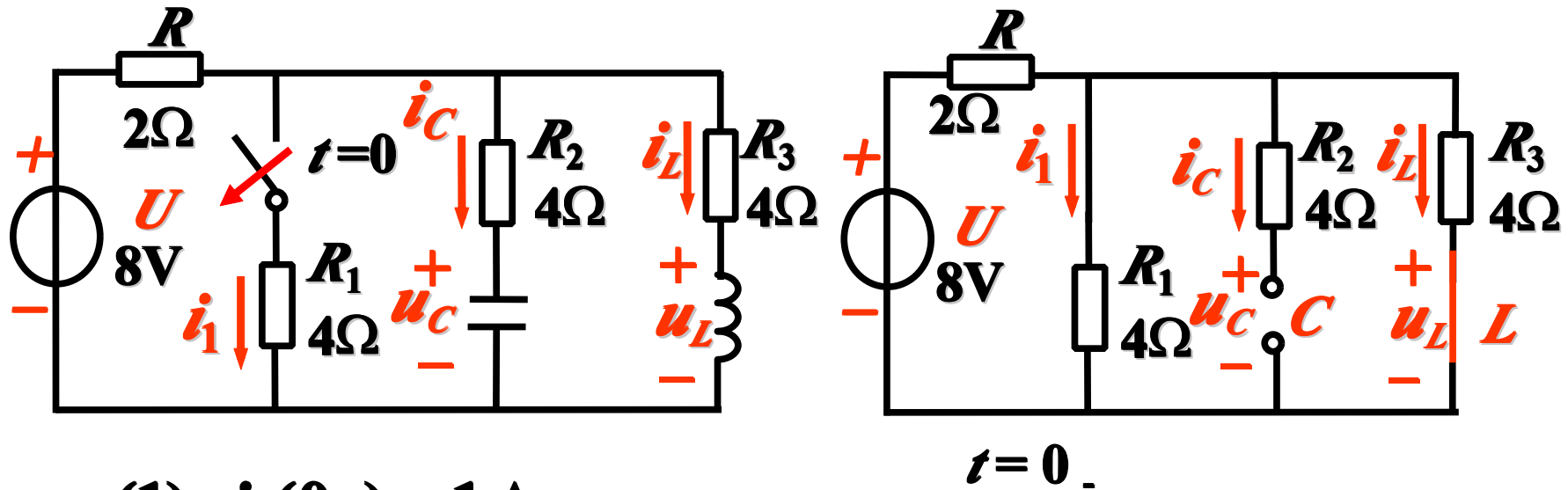


$$(1) \quad i_L(0_-) = 1 \text{ A}$$

$$u_C(0_-) = R_3 i_L(0_-) = 4 \times 1 = 4 \text{ V}$$

$$i_L(0_+) = i_L(0_-) = 1 \text{ A}$$

$$u_C(0_+) = u_C(0_-) = 4 \text{ V}$$

2

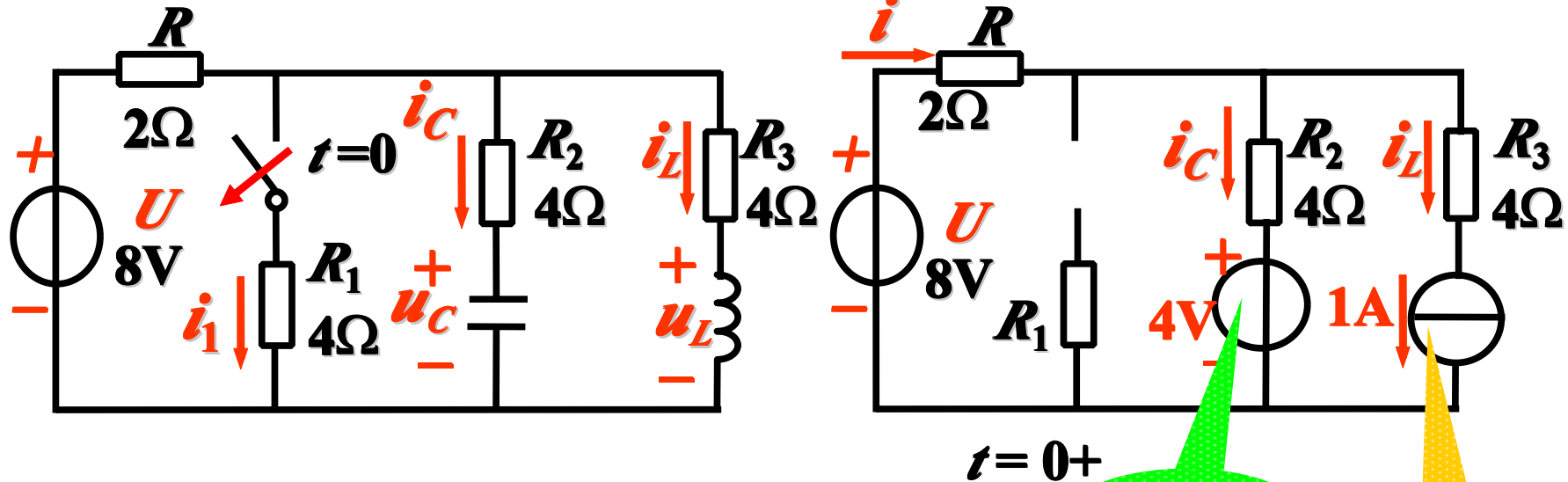

(2) $t = 0_+$

$i_C(0_+)$

$u_L(0_+)$

$u_C(0_+)$

$i_L(0_+)$



$$U = Ri(0_+) + R_2 i_C(0_+) + u_C(0_+)$$

$$i(0_+) = i_C(0_+) + i_L(0_+)$$

$$8 = 2i(0_+) + 4i_C(0_+) + 4$$

$$i(0_+) = i_C(0_+) + 1$$


2

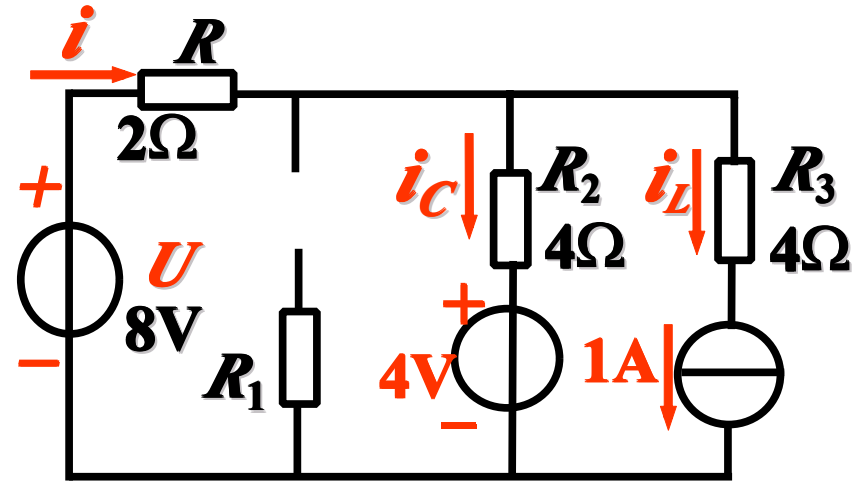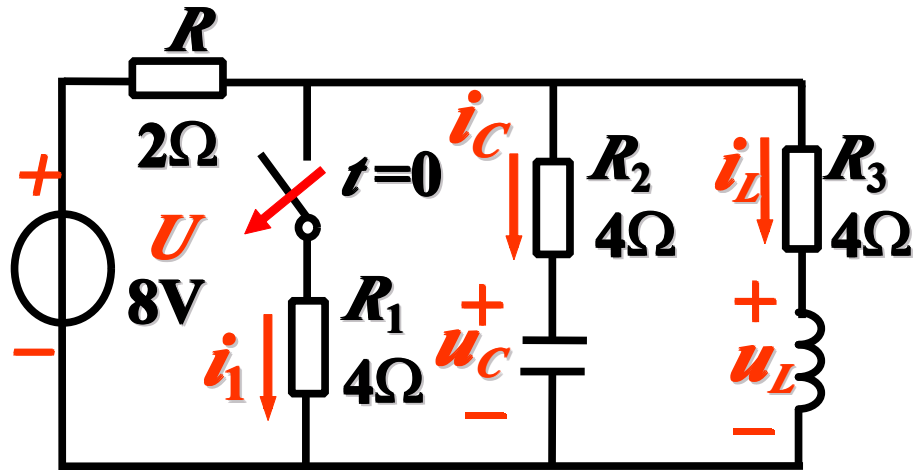

$t = 0+$

$$i_C(0_+) = \frac{1}{3} \text{ A}$$
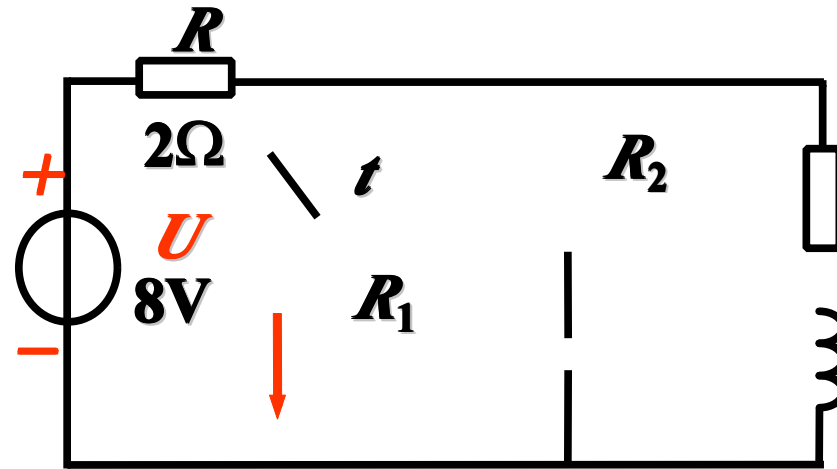
$$\begin{aligned} u_L(0_+) &= R_2 i_C(0_+) + u_C(0_+) - R_3 i_L(0_+) \\ &= 4 \times \frac{1}{3} + 4 - 4 \times 1 = 1\frac{1}{3} \text{ V} \end{aligned}$$



	u_C / V	i_L / A	i_C / A	u_L / V
$t=0_-$	4	1	0	0
$t=0_+$	4	1	$\frac{1}{3}$	$1\frac{1}{3}$

u_C i_L

i_C u_L



1. u_C i_L ,

2. , , ($t=0_+$
)

3. , $u_C(0^-) \neq 0$ $i_L(0^-) \neq 0$ ($t=0_+$
)

$u_C(0_+)$;

$i_L(0_+)$

3.2



,

1.

:

(

)

(


)

2.

{

3.2.1 RC

RC

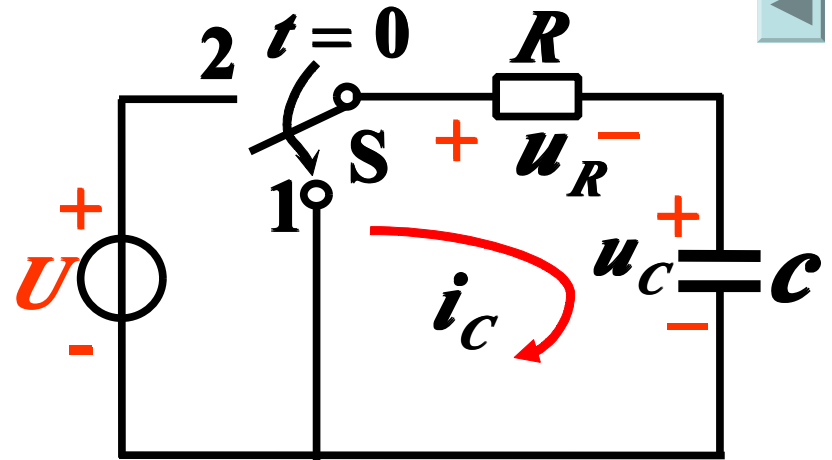

$$u_C(0_-) = U$$

$$u_C(0_-) = U$$

$t=0$ S \rightarrow 1,

C R

1. u_C ($t \geq 0$)


(1) KVL

$$= i$$

$$+ = 0$$

$$i = \frac{d}{d}$$

$$\frac{d}{d} + = 0$$

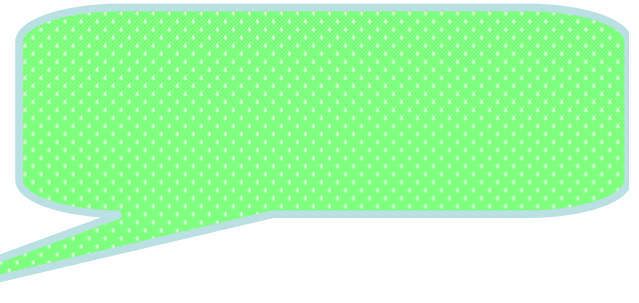

(2)

$$RC \frac{du_C}{dt} + u_C = 0 \quad : u_C = Ae^{pt}$$
$$+ 1 = 0 \quad \therefore = -\frac{1}{RC}$$

$$u_C = Ae^{-\frac{t}{RC}}$$

A

$$t = (0_+) \quad u_C(0_+) = U, \quad A = U$$

(3)

u_C

$$u_C = U e^{-\frac{t}{RC}} = u_C(0_+) e^{-\frac{t}{\tau}} \quad t \geq 0$$

u_C
RC




2.

$$u_C = U e^{-\frac{t}{RC}}$$

$$i_C = C \frac{du_C}{dt} = -\frac{U}{R} e^{-\frac{t}{RC}}$$

$$u_R = i_C R = -U e^{-\frac{t}{RC}}$$

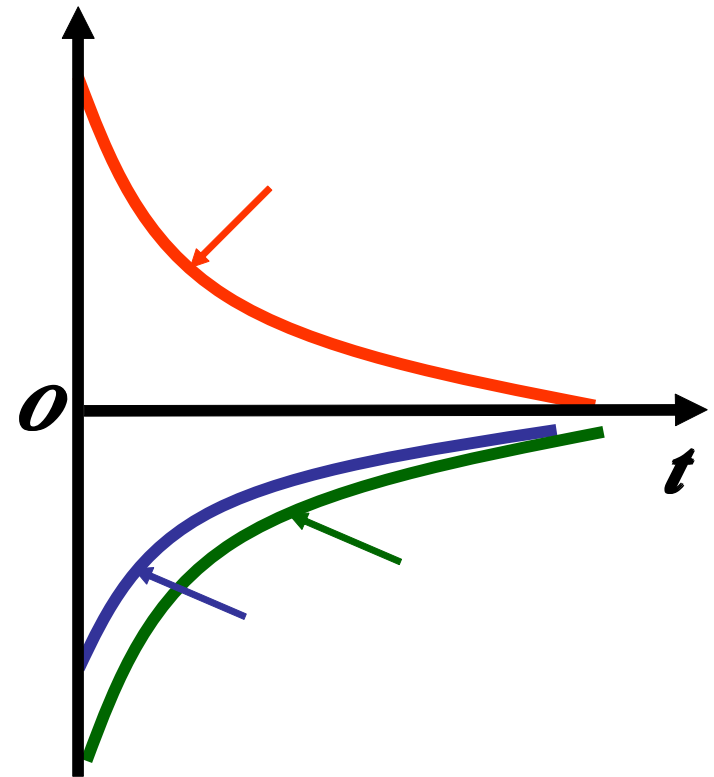

3.



4.

: $\tau = RC$: S



(1) $\Omega \frac{A \cdot s}{V} = S$

τ

(2)

$$u_C(t) = U e^{-\frac{t}{RC}}$$

$$t = \tau \quad = e^{-1} = 36.8\%$$

\therefore

τ

u_C

U_0

36.8%

(3)



$$t \rightarrow \infty \quad u_C \rightarrow 0$$

$$\underline{t = (3 \sim 5)\tau} \quad u_C \rightarrow 0$$

$$e^{-\frac{t}{\tau}}$$


t	τ	2τ	3τ	4τ	5τ	6τ
$e^{-\frac{t}{\tau}}$	e^{-1}	e^{-2}	e^{-3}	e^{-4}	e^{-5}	e^{-6}
u_C	$0.368U$	$0.135U$	$0.050U$	$0.018U$	$0.007U$	$0.002U$

$$t=5\tau$$

$$u_C$$

3.2.2 *RL*

1. *RL*

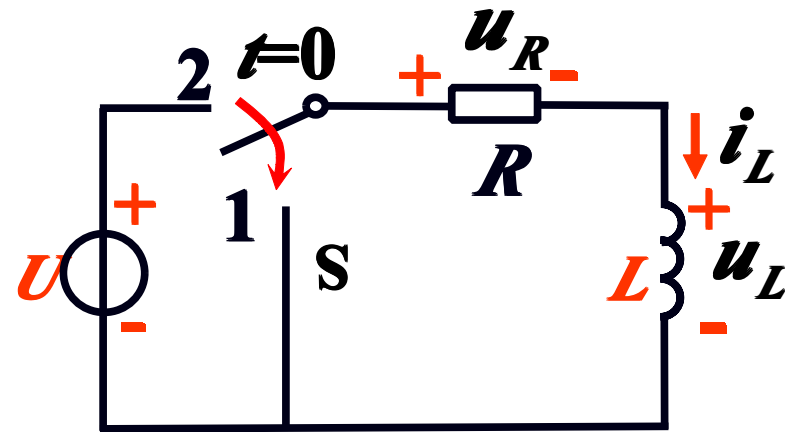

$$(0_-) = \text{---}$$

$t=0$

, L R

(1) i_L

1) KVL

$$= i$$

$$+ = 0$$

$$= \frac{d}{d}$$

$$-\frac{d}{d} + = 0$$





(2)


$$= -e^{-\frac{t}{\tau}}$$

$$= \frac{d}{dt} = -e^{-\frac{t}{\tau}}$$

$$= e^{-\frac{t}{\tau}}$$

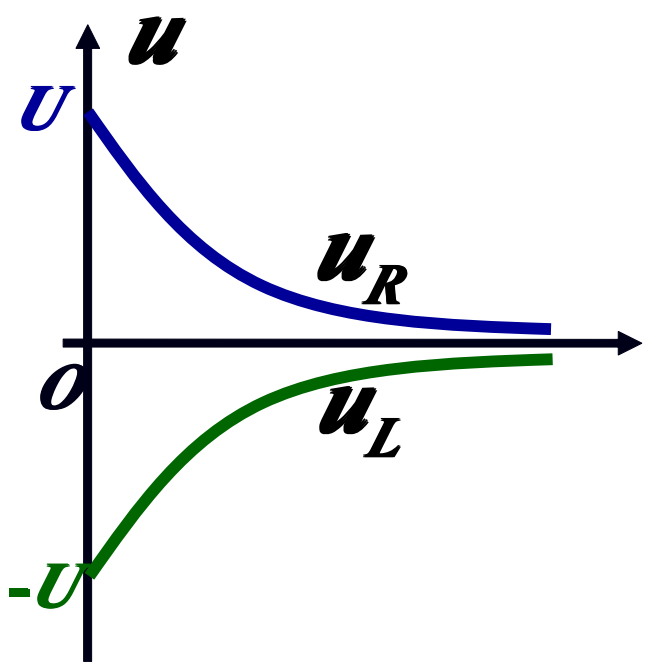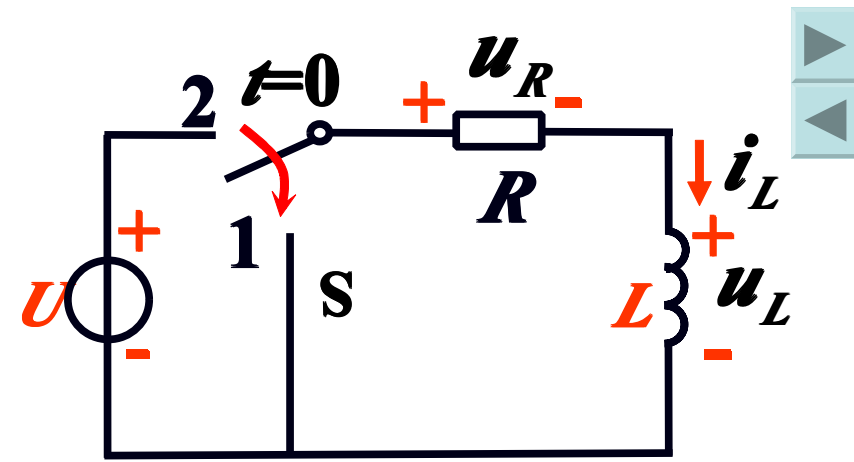

(3)

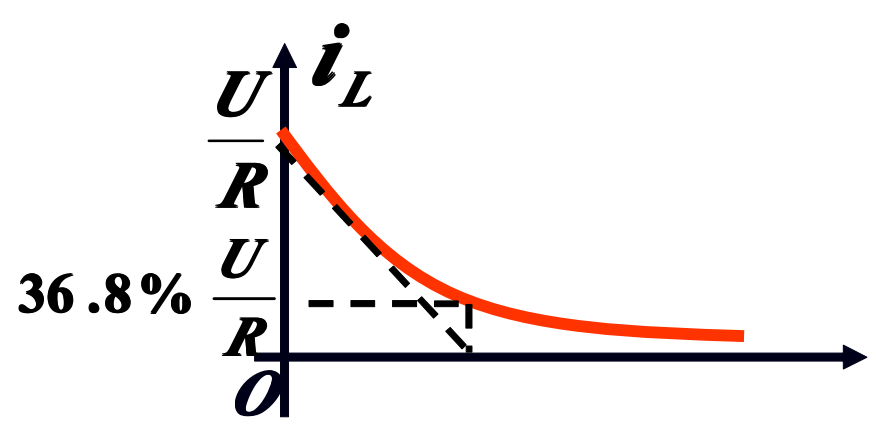

(4)

$$\tau = \frac{L}{R}$$

2. *RL*

(1)

1)



$$\therefore i_L(0_-) = \frac{U}{R}$$

$$i_L(0_+) = 0 \quad \therefore u_L = -e_L = L \frac{di}{dt} \rightarrow \infty$$

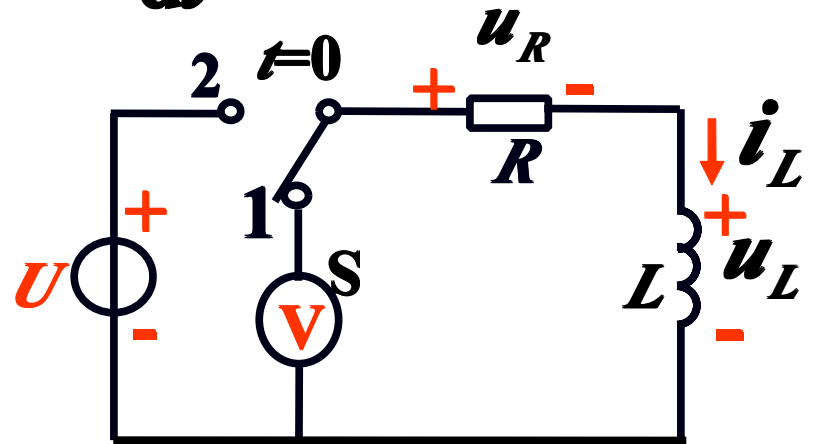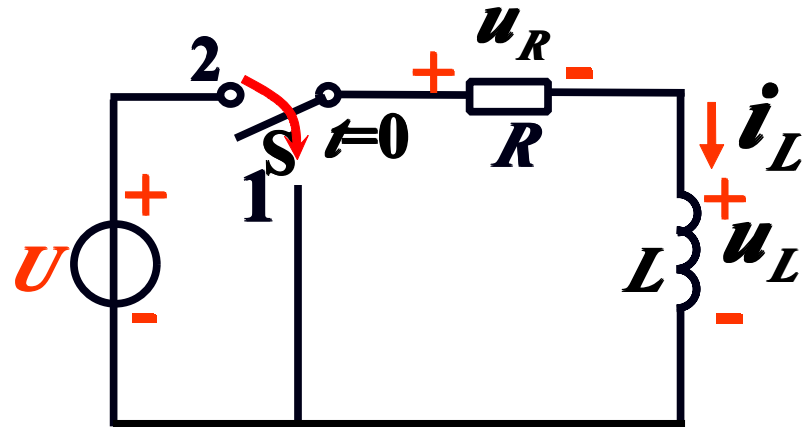2)

$$\therefore i_L(0_+) = i_L(0_-) = \frac{U}{R}$$

$$V(0_+) = i_L(0_+) \times R = \frac{U}{R} \times R$$






(2)


1)

R'

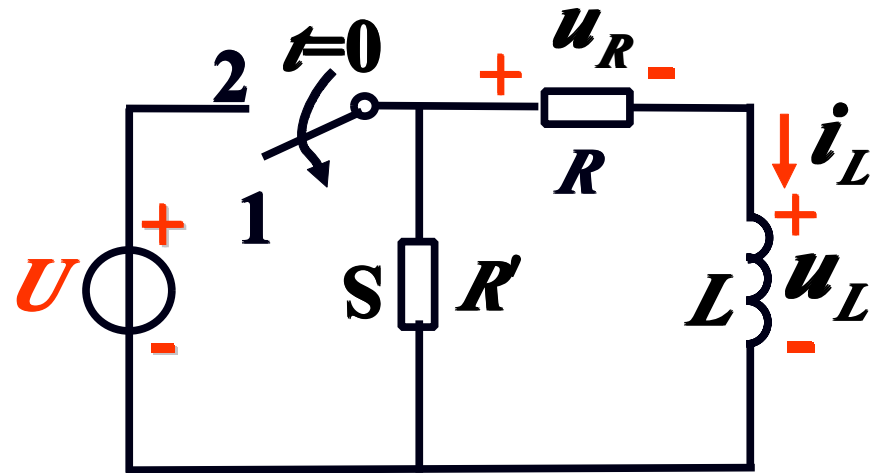

2)

V_D

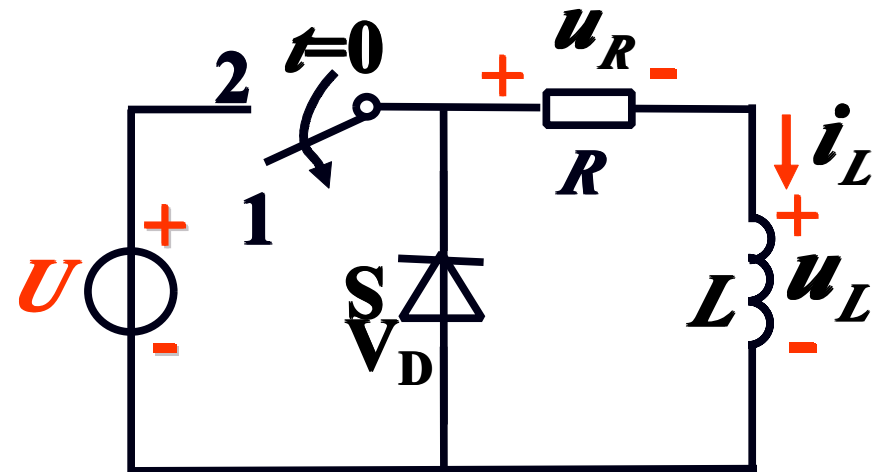


3.3

3.3.1 RC

RC


$t = 0$

S

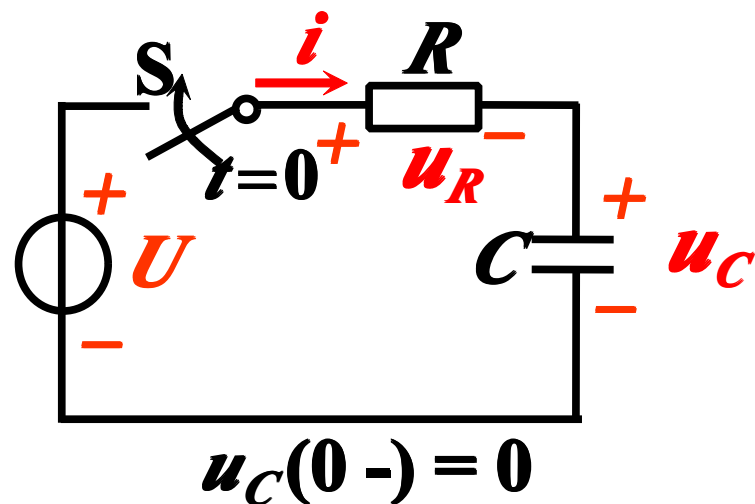

,
 u

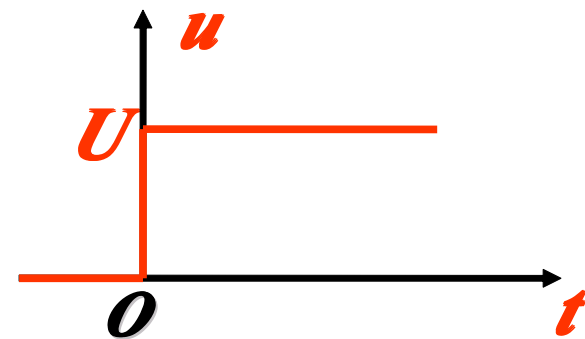
$$u = \begin{cases} 0 & t < 0 \\ U & t \geq 0 \end{cases}$$



1. u_C

(1) KVL $u_R + u_C = U$

$$RC \frac{du_C}{dt} + u_C = U$$

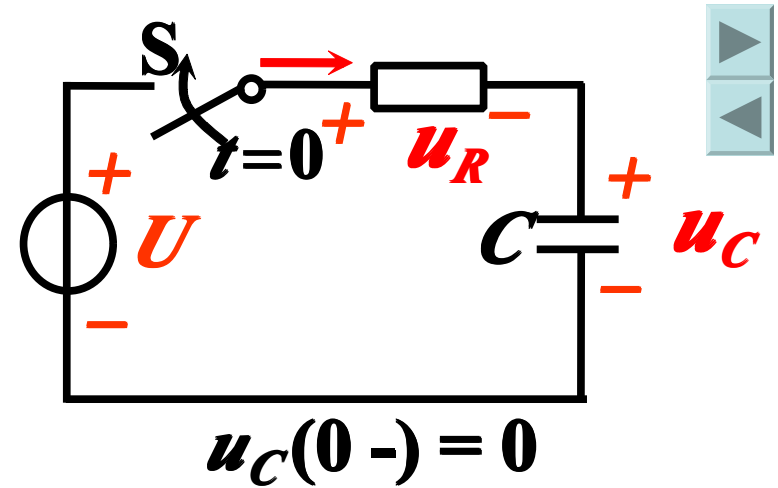

$$= +$$
$$u_C(t) = u'_C + u''_C$$

(2)

$$RC \frac{du_C}{dt} + u_C = U$$

$$u'_C = K, \quad U = RC \frac{dK}{dt} + K$$

$$K = U, \quad u'_C = U$$

$$\therefore u_C = u'_C + u''_C = U + Ae^{-\frac{t}{RC}}$$

$$u'_C$$

$$u'_C(t) = u_C(\infty) = U$$

$$RC \frac{du_C}{dt} + u_C = 0$$

$$u''_C = Ae^{pt} = Ae^{-\frac{t}{RC}}$$

$$u_C = u'_C + u''_C = U + Ae^{-\frac{t}{\tau}} \quad \tau = RC$$

A

$t=0_+$

$$u_C(0_+) = 0$$


$$A = -U$$



(3)

u_C

$$u_C = U - Ue^{-\frac{t}{RC}}$$

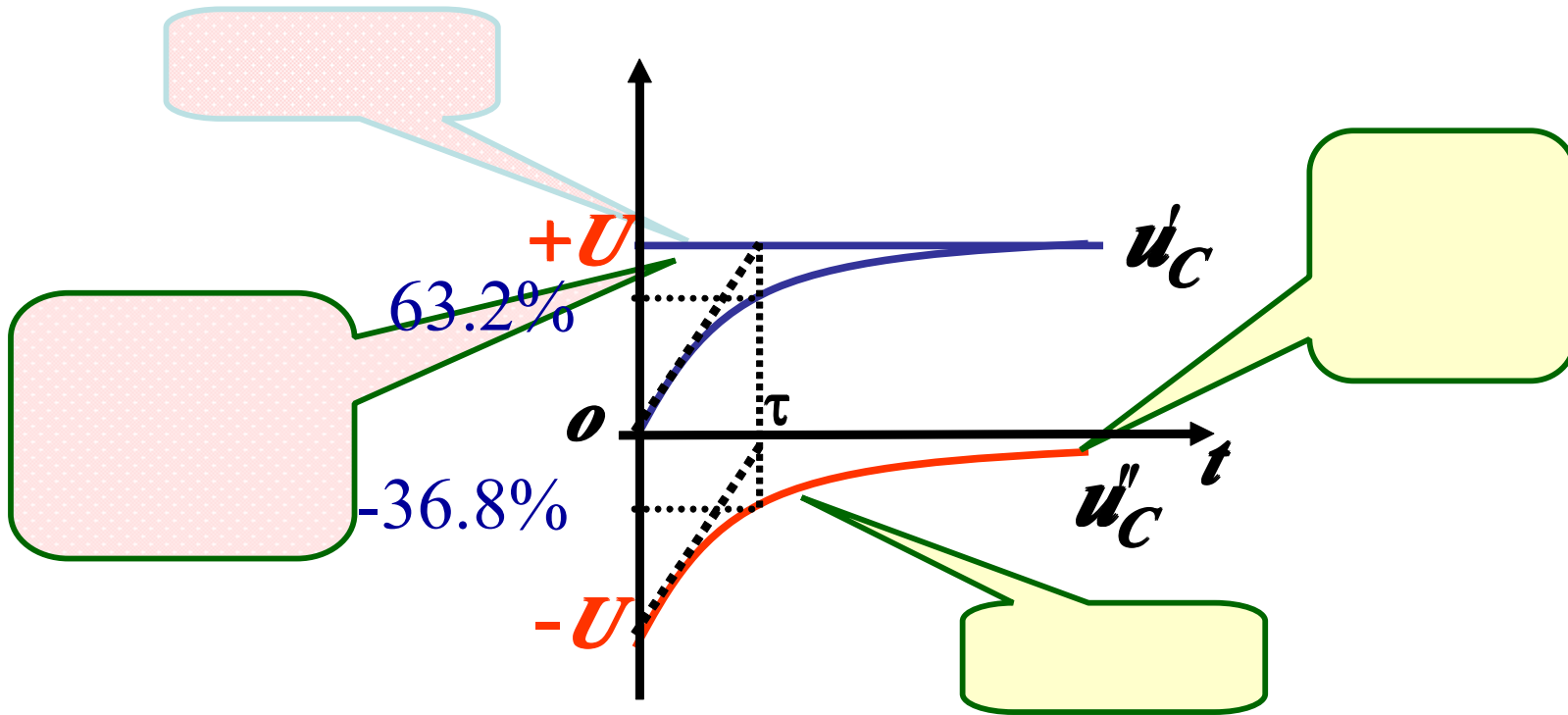



2. i_C

$$i_C = C \frac{du_C}{dt} = \frac{U}{R} e^{-\frac{t}{\tau}} \quad t \geq 0$$

$t = 0$

3. u_C i_C

$$u_C = U(1 - e^{-\frac{t}{RC}})$$

4. τ


$t = \tau$

$$u_C(\tau) = U(1 - e^{-1}) = 63.2\%U$$


τ

63.2%

u_C

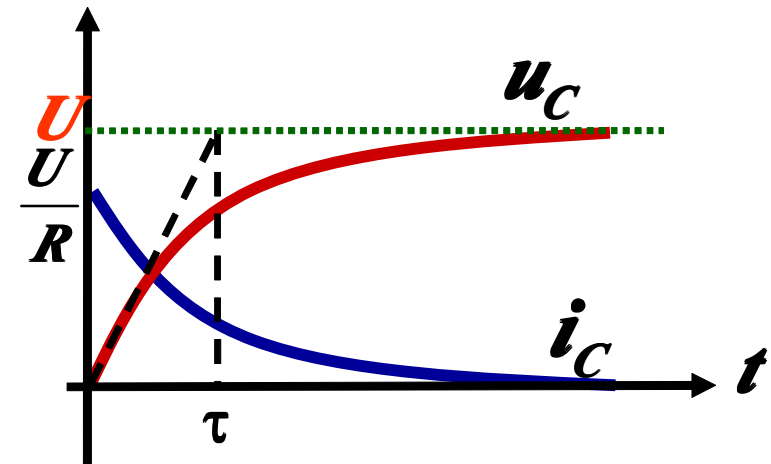

	0	τ	2τ	3τ	4τ	5τ	6τ
u_C	0	$0.632U$	$0.865U$	$0.950U$	$0.982U$	$0.993U$	$0.998U$

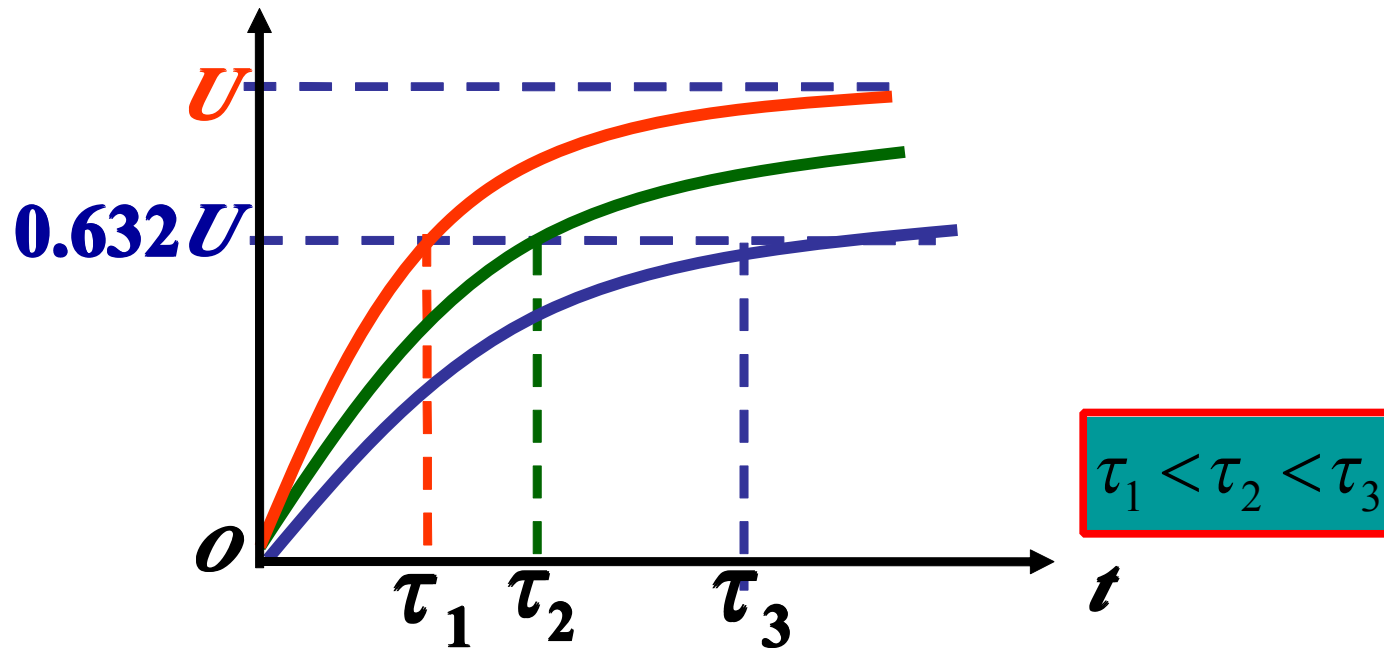

τ

u_C

$t = 5\tau$,

u_C

3.3.2 *RL*

1. i_L

(1) KVL


$$-\frac{d}{d} + = -$$

$$= +$$

$$() = ' + ''$$

(2)

$$() = (\infty) = -$$

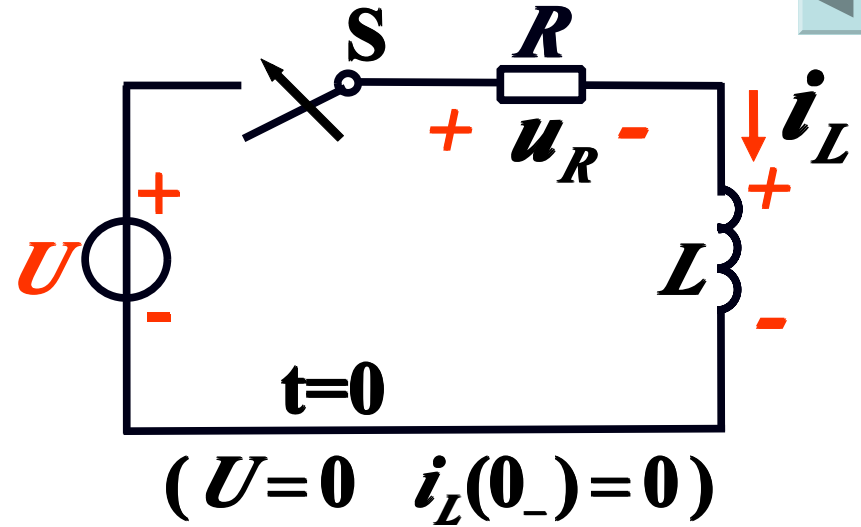





$$i_L = \frac{U}{R} (1 - e^{-\frac{R}{L}t})$$

$$u_L = L \frac{di}{dt} = U e^{-\frac{t}{\tau}} = U e^{-\frac{R}{L}t}$$

$$u_R = i_L R = U (1 - e^{-\frac{R}{L}t})$$



2. i_L u_L u_R

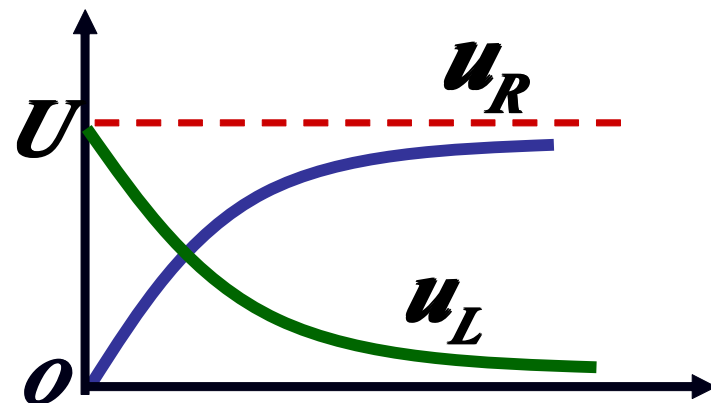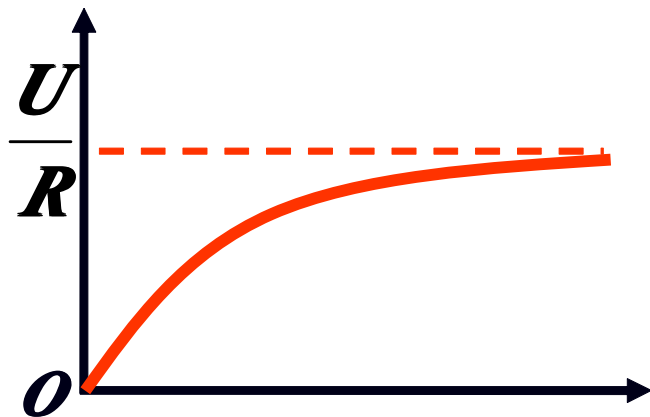


3.4



1.

$$RC \frac{du_C}{dt} + u_C = U_S$$

$$u_C(0_+) = u_C(0_-) = U_0$$

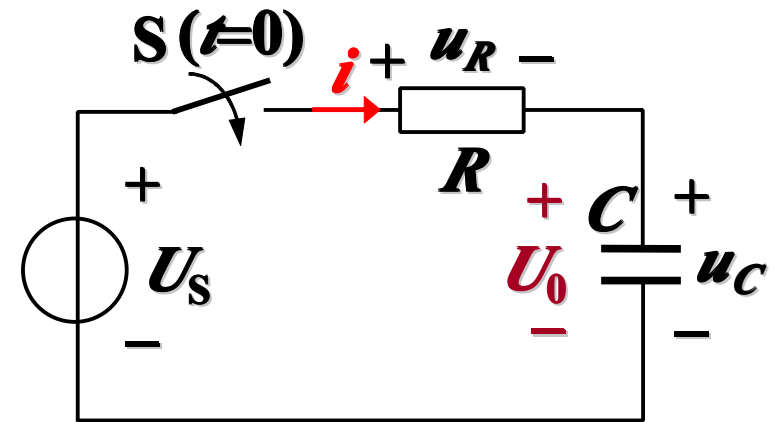

2.

$$u_C = U_S + (U_0 - U_S) e^{-\frac{t}{\tau}}$$




(1)





()
()

$$u_C = U_S + (U_0 - U_S) e^{-\frac{t}{\tau}}$$

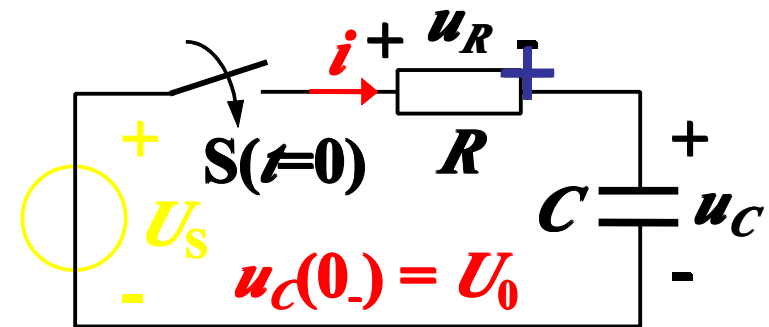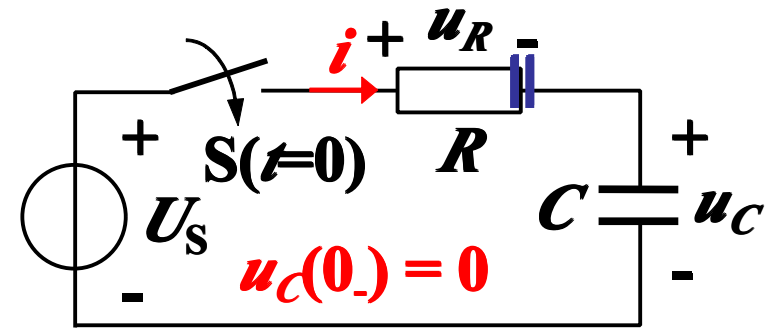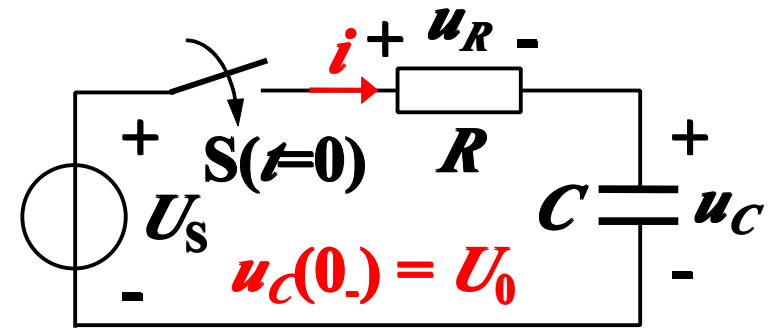
(2)

$$u_C = U_S (1 - e^{-\frac{t}{\tau}}) + U_0 e^{-\frac{t}{\tau}}$$



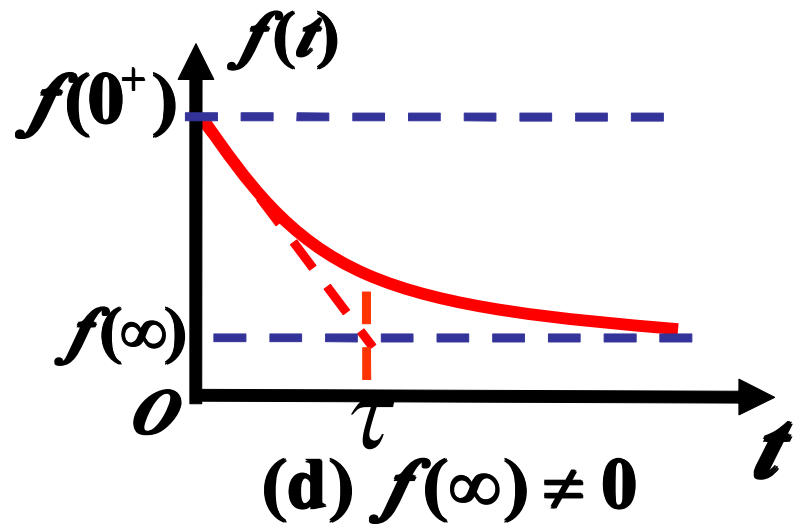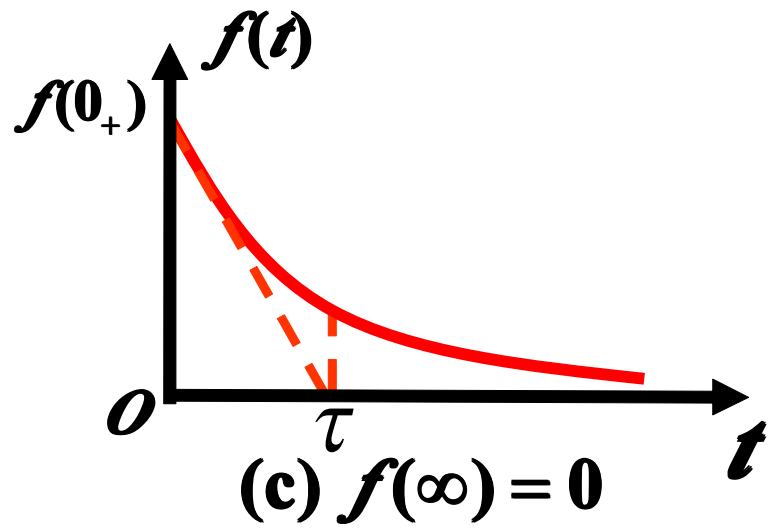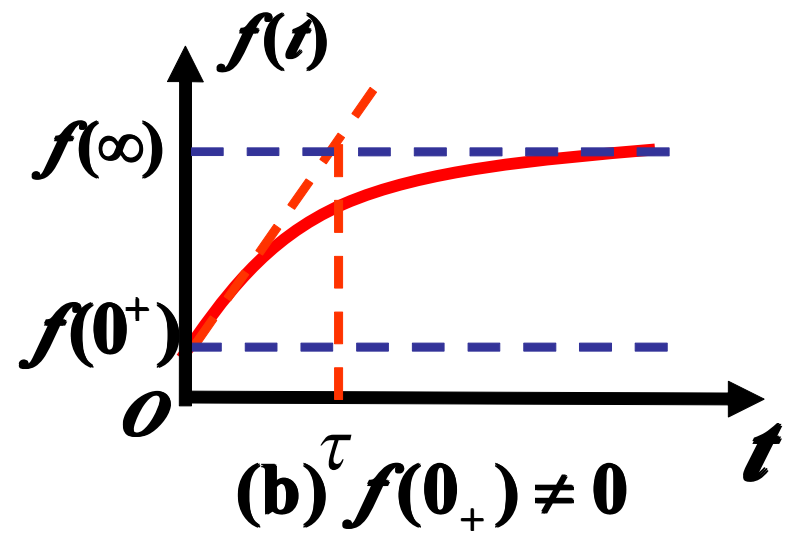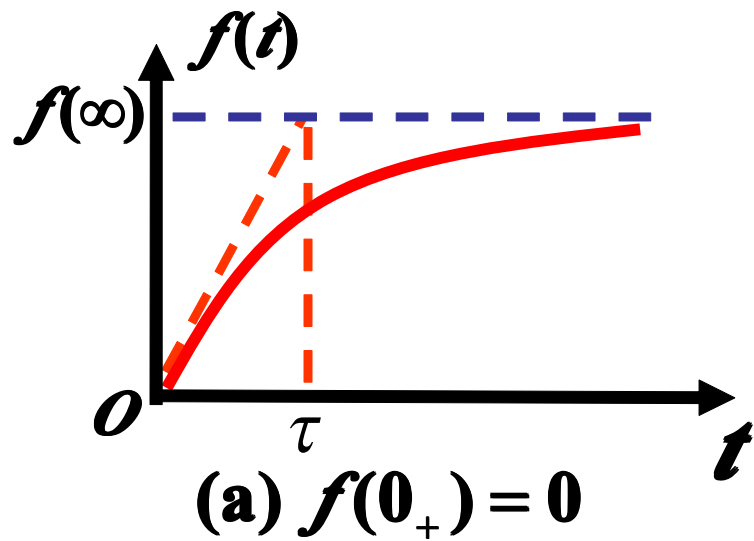

3.5

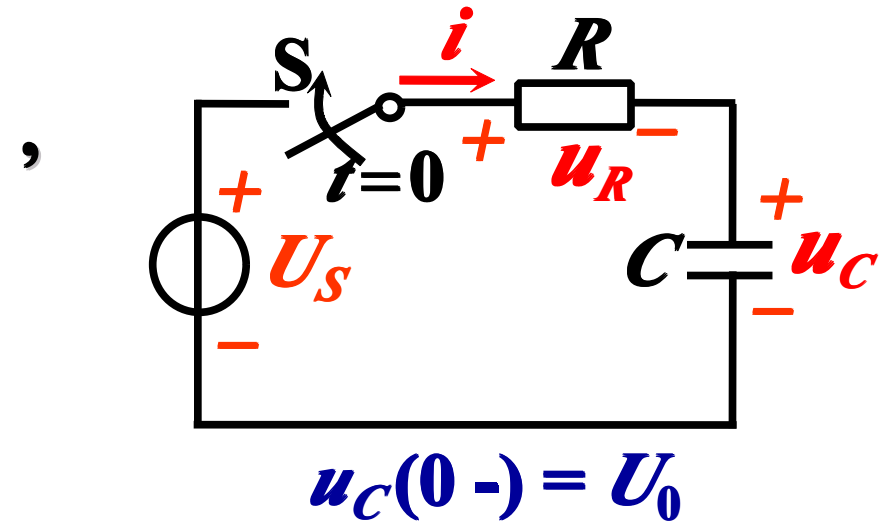

$$= \underline{\quad} + (\underline{u_C(0^-)} - \underline{\quad}) e^{-\frac{t}{\tau}}$$

$$(\infty) = \underline{\quad}$$

$$(0_+) = \underline{u_C(0_-)} = \underline{U_0}$$

$$\underline{u_C} = \underline{u_C(\infty)} + [\underline{u_C(0_+)} - \underline{u_C(\infty)}] e^{-\frac{t}{RC}}$$



$$f(t) = f(\infty) + [f(0_+) - f(\infty)] e^{-t/\tau}$$

, $f(t)$

$$\left\{ \begin{array}{l} f(0_+) \text{ ---} \\ f(\infty) \text{ ---} \\ \tau \text{ ---} \end{array} \right.$$

τ

()







(2) $f(0_+)$

1) $t=0_-$ $u_C(0_-)$ $i_L(0_-)$

2) $\left\{ \begin{array}{l} u_C(0_+) = u_C(0_-) \\ i_L(0_+) = i_L(0_-) \end{array} \right.$

3) $t=0_+$ $u(0_+)$ $i(0_+)$

(3) τ

RC

$$\tau = R_0 C$$

RL

$$\tau = \frac{L}{R_0}$$

1)

$$R_0 = R;$$

2)


$$R_0$$



 R_0



$$R_0 = (R_1 // R_2) + R_3$$

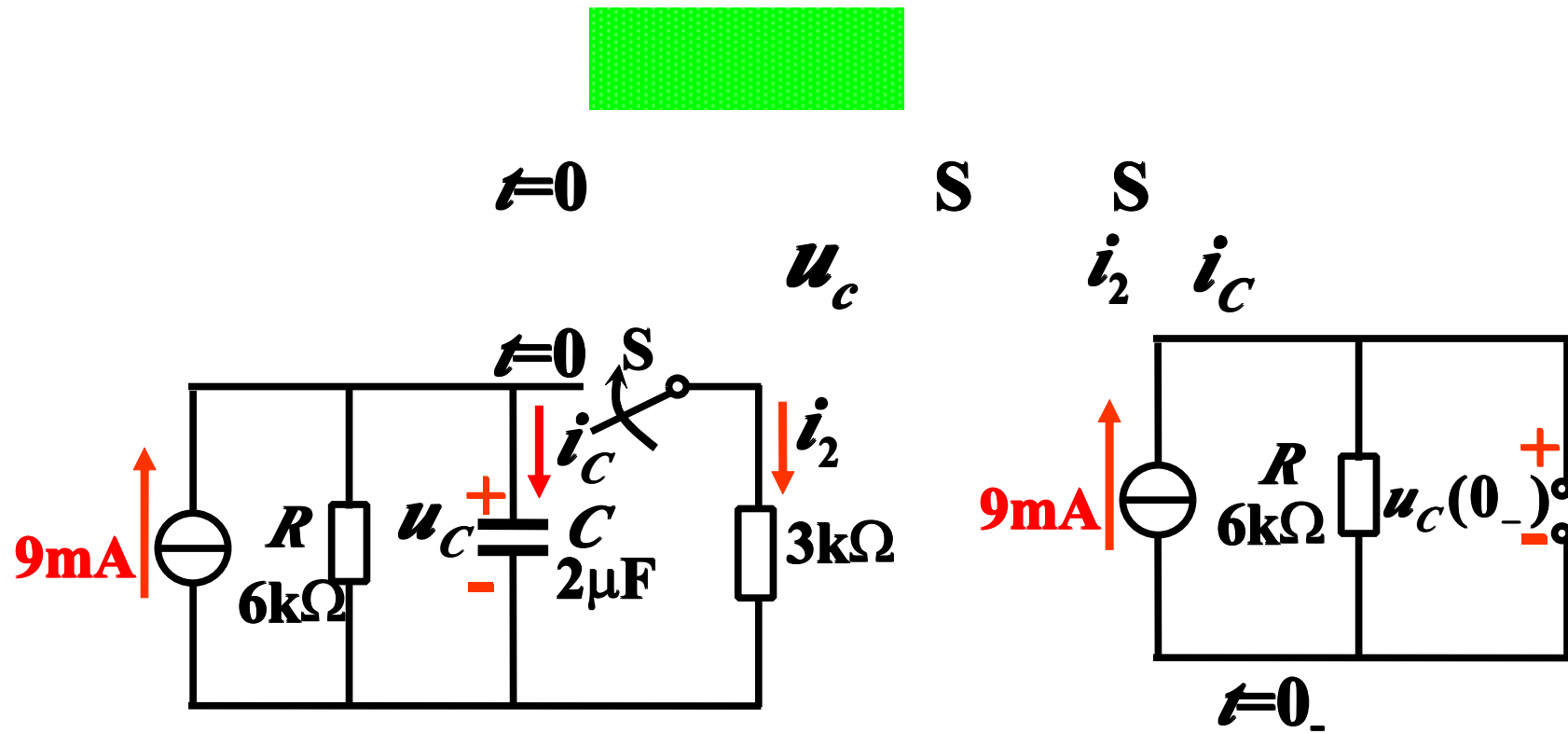

$$u_C = u_C(\infty) + [u_C(0_+) - u_C(\infty)] e^{-\frac{t}{\tau}}$$

(1)

$$u_C(0_+) = u_C(0_-) = 9 \times 10^{-3} \times 6 \times 10^3 = 54 \text{ V}$$
$$u_C(0_+) = u_C(0_-) = 54 \text{ V}$$



(2)

$u_c(\infty)$


$u_c(\infty)$


$$u_c(\infty) = 9 \times 10^{-3} \times \frac{6 \times 3}{6 + 3} \times 10^3$$
$$= 18 \text{ V}$$

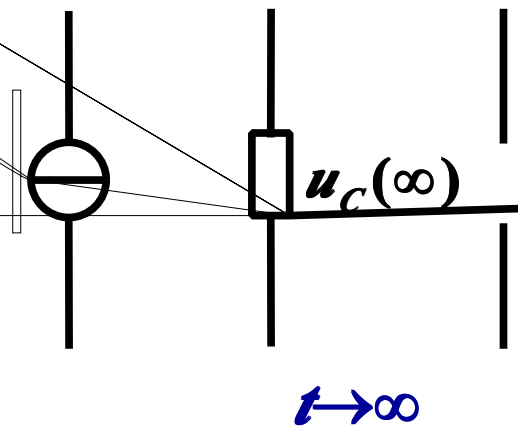(3)


τ

$$\tau = R_0 C$$
$$= \frac{6 \times 3}{6 + 3} \times 10^3 \times 2 \times 10^{-6}$$
$$= 4 \times 10^{-3} \text{ s}$$



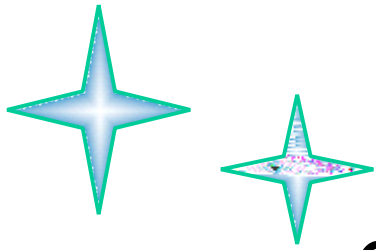
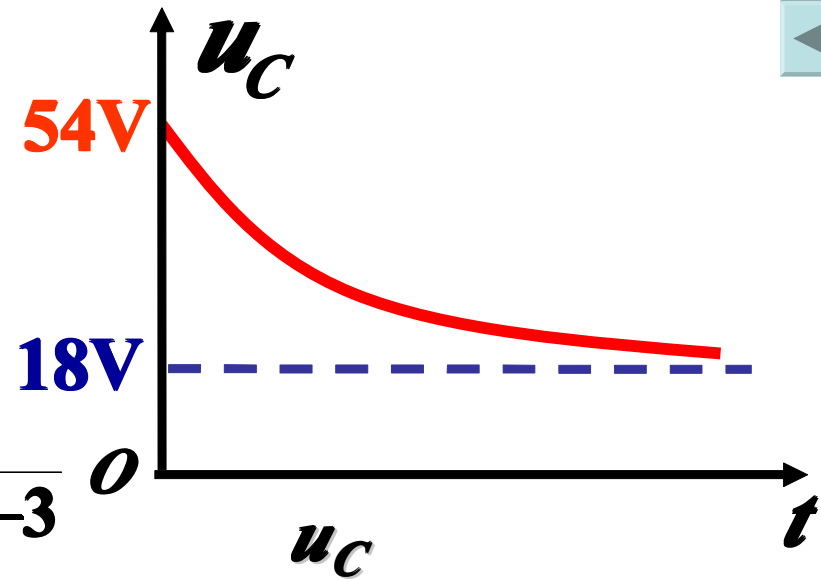
$$\begin{cases} u_C(0_+) = 54 \text{ V} \\ u_C(\infty) = 18 \text{ V} \\ \tau = 4 \times 10^{-3} \text{ s} \end{cases}$$





$$\begin{aligned} \therefore u_C &= 18 + (54 - 18)e^{-\frac{t}{4 \times 10^{-3}}} \\ &= 18 + 36e^{-250t} \text{ V} \end{aligned}$$

u_C
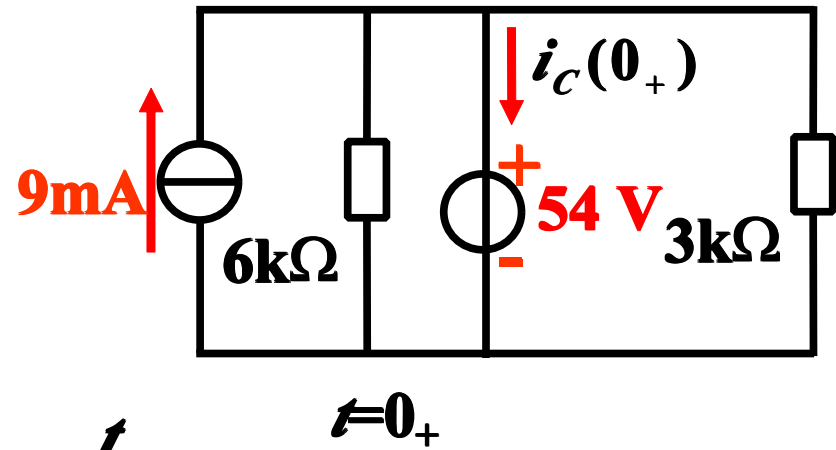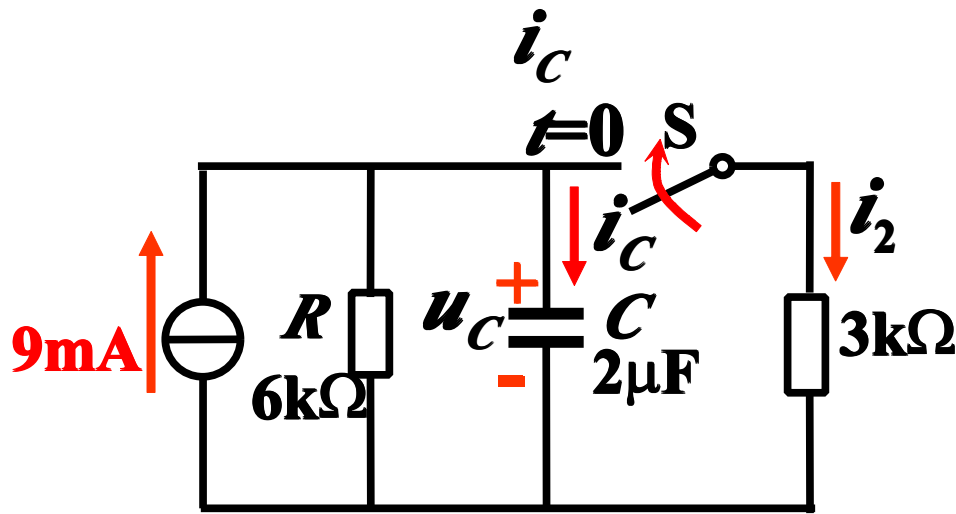
$$\begin{aligned} i_C &= C \frac{du_C}{dt} = 2 \times 10^{-6} \times 36 \times (-250)e^{-250t} \\ &= -0.018e^{-250t} \text{ A} \end{aligned}$$






$$i_c = i_c(\infty) + [i_c(0_+) - i_c(\infty)] e^{-\frac{t}{\tau}}$$

$$i_c(0_+) = \frac{18 - 54}{2 \times 10^3} = -18 \text{ mA}$$

$$i_c(\infty) = 0$$

$$i_c(t) = -18 e^{-250t} \text{ mA}$$
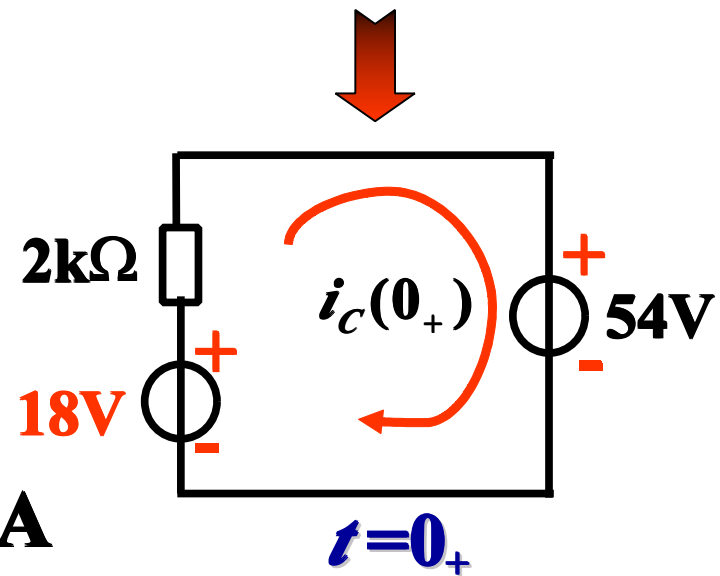
$$i_2(t) = \frac{u_c(t)}{3 \times 10^3} = 6 + 12 e^{-250t} \text{ mA}$$



2

S



$t=0$ S
 i_1 i_2



$t=0$



u_C i_C

$u_C(0_+)$
 $t=0-$

$$u_C(0_-) = \frac{6}{1+2+3} \times 3 = 3 \text{ V}$$

$$u_C(0_+) = u_C(0_-) = 3 \text{ V}$$

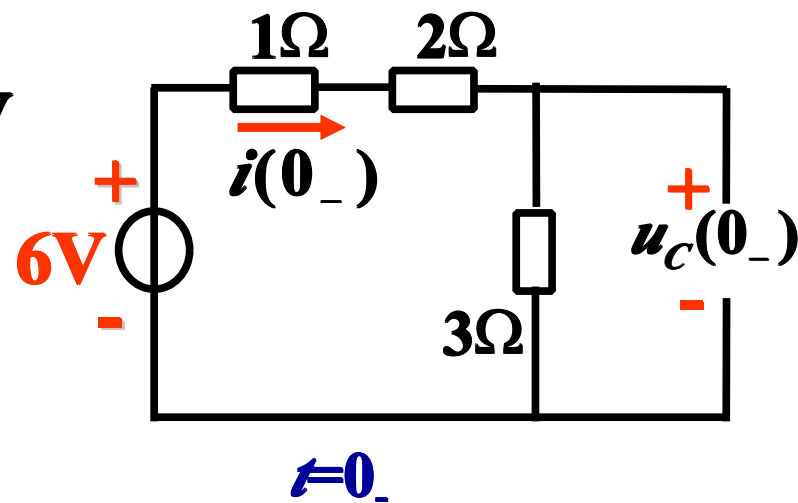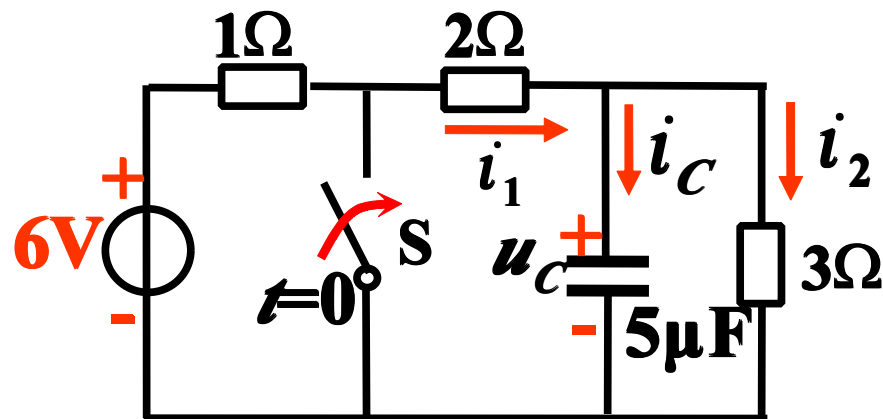

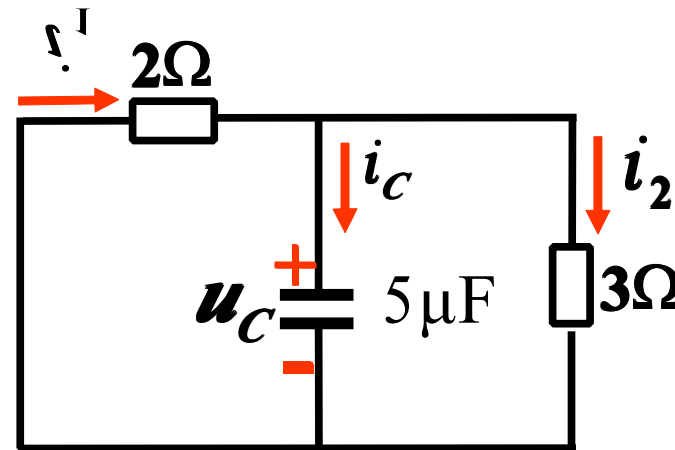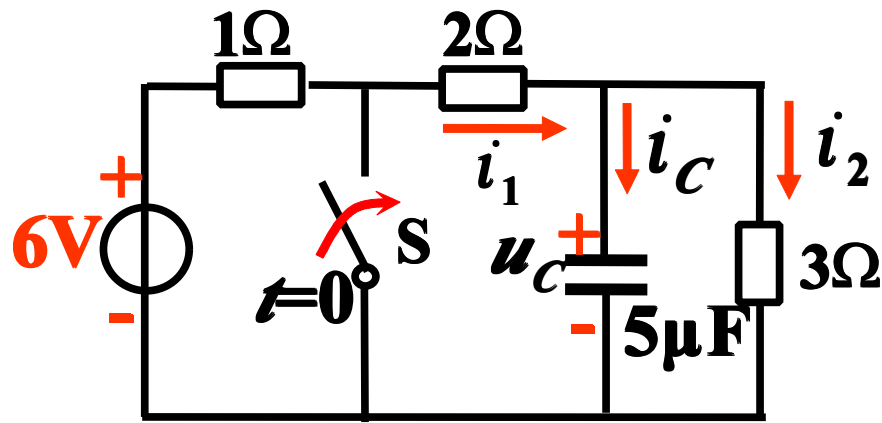

$$u_C(\infty) \quad u_C(\infty) = 0$$



τ

$$\tau = R_0 C = \frac{2 \times 3}{2 + 3} \times 5 \times 10^{-6} = 6 \times 10^{-6} \text{ s}$$

$$\begin{aligned} \therefore u_C(t) &= u_C(\infty) + [u_C(0_+) - u_C(\infty)] U e^{-\frac{t}{\tau}} \\ &= 0 + 3e^{-\frac{10^6}{6}t} = 3e^{-1.7 \times 10^5 t} \text{ V} \end{aligned}$$

3

$t=0$

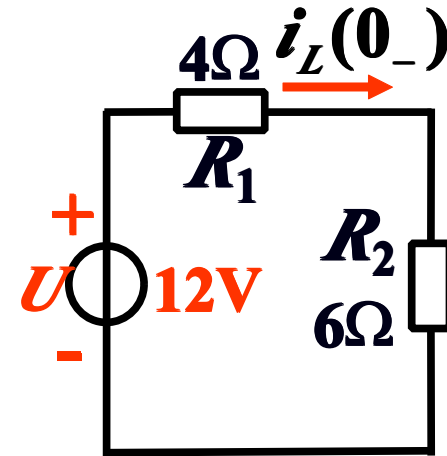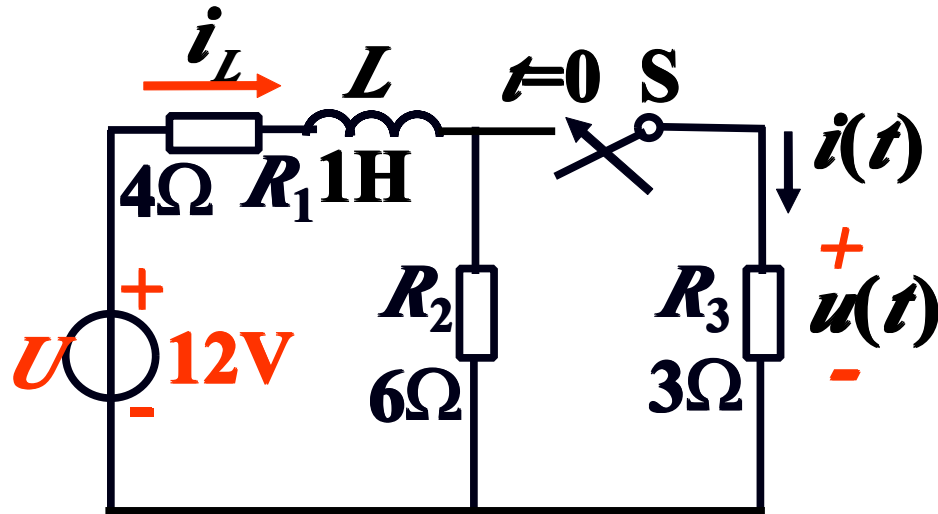

$t=0_-$

1. i_L ()

$$i_L = i_L(\infty) + [i_L(0_+) - i_L(\infty)] e^{-\frac{t}{\tau}}$$

$$i_L(0_+) = i_L(0_-) = \frac{U}{R_1 + R_2} = \frac{12}{4 + 6} = 1.2 \text{ A}$$

$$i_L(\infty) = \frac{U}{R_1 + \frac{R_2 \times R_3}{R_2 + R_3}}$$



$$= 2 \text{ A}$$

$$\tau = \frac{L}{R_0}$$

$$= \frac{L}{R_1 + \frac{R_2 \times R_3}{R_2 + R_3}}$$

$$= \frac{1}{6} \text{ s}$$
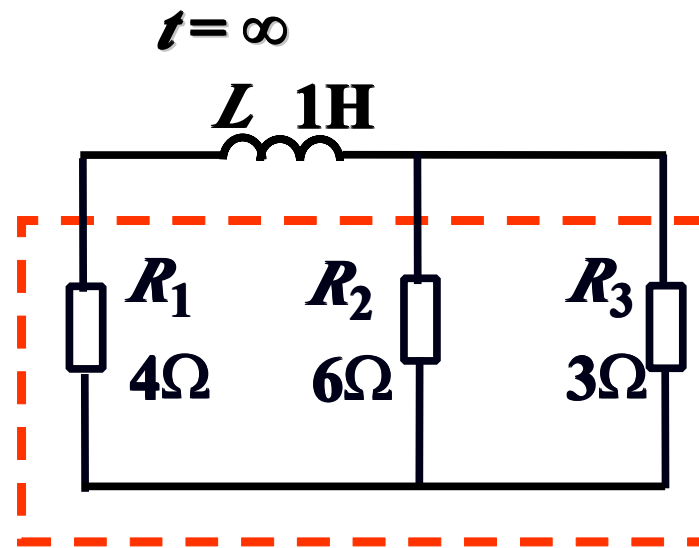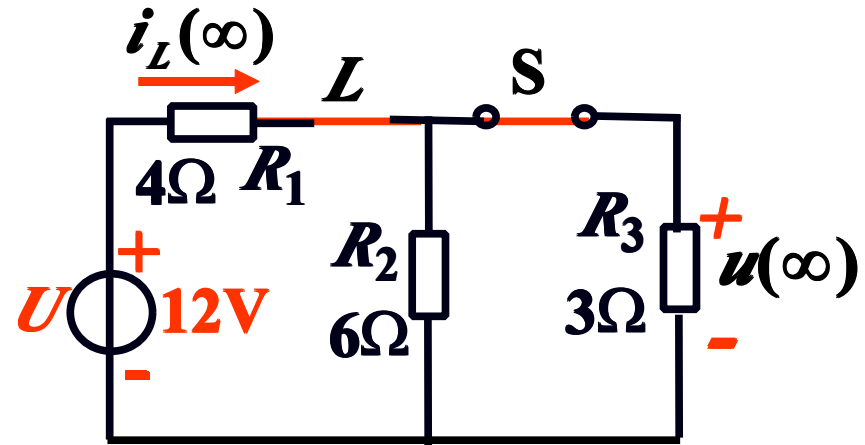
$$\therefore i_L = 2 + (1.2 - 2)e^{-6t} = 2 - 0.8e^{-6t} \quad (t \geq 0)$$



2. $u(t)$


$$u = iR_3 = \frac{R_2}{R_2 + R_3} \times i_L \times R_3$$

$$u = \frac{6 \times 3}{6 + 3} (2 - 0.8e^{-6t}) = 4 - 1.6e^{-6t} \text{ V } (t \geq 0)$$

u

$$u = u(\infty) + [u(0_+) - u(\infty)] e^{-\frac{t}{\tau}}$$
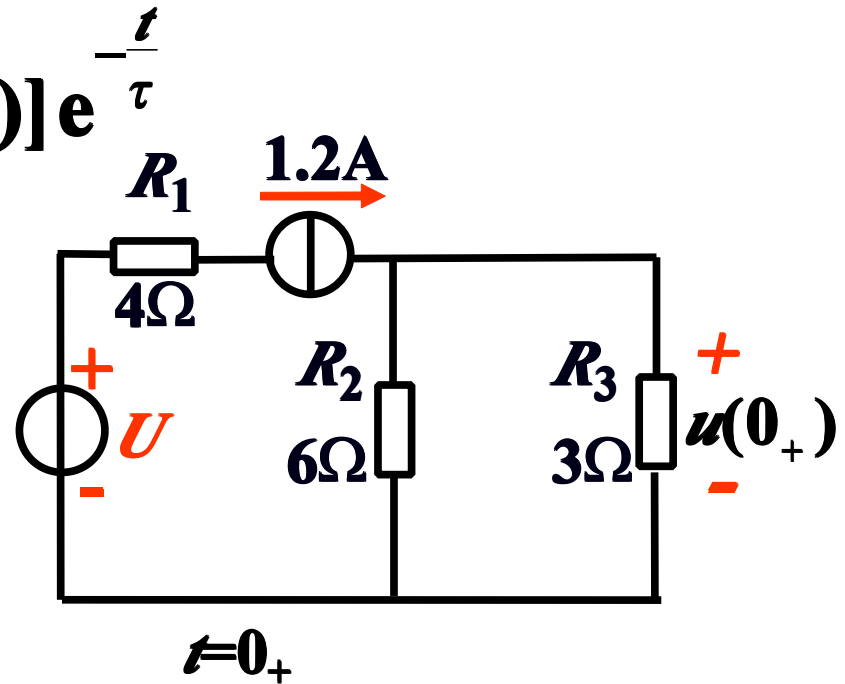
$$\begin{aligned} u(0_+) &= \frac{6}{6+3} \times 1.2 \times R_3 \\ &= \frac{2}{3} \times 1.2 \times 3 = 2.4 \text{ V} \end{aligned}$$





$$\begin{aligned} u_L(\infty) &= \frac{R_2}{R_2 + R_3} i_L(\infty) \times R_3 \\ &= \frac{6}{9} \times 2 \times 3 = 4 \text{ V} \\ \tau &= \frac{L}{R} = \frac{1}{6} \text{ s} \\ u_L(t) &= (2.4 - 4)e^{-6t} \\ &= -1.6e^{-6t} \text{ V} \quad (t \geq 0) \end{aligned}$$




4:

S $t=0$

:

i_L

u_L

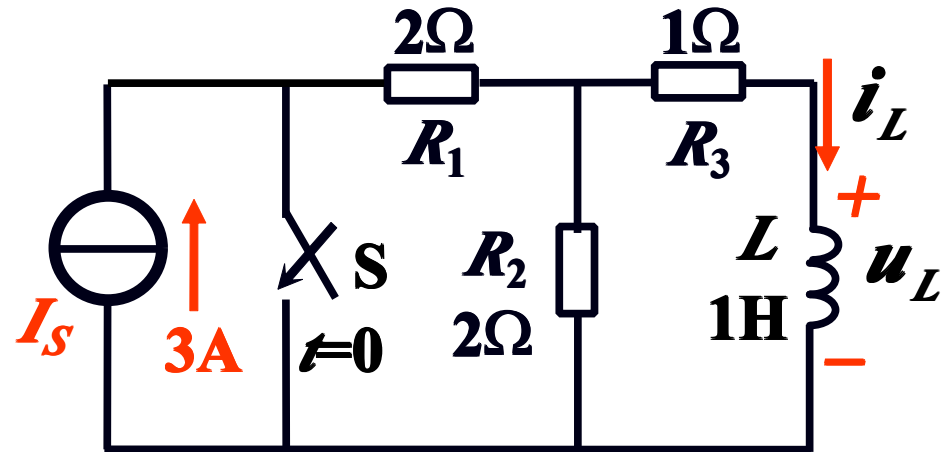


:


(1) $u_L(0_+)$, $i_L(0_+)$

$t=0^-$

$$i_L(0_-) = \frac{2}{1+2} \times 3 = 2 \text{ A}$$

$$i_L(0_+) = i_L(0_-) = 2 \text{ A}$$

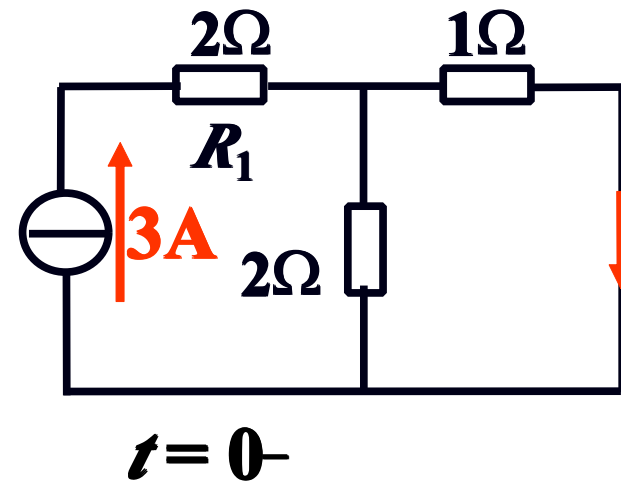

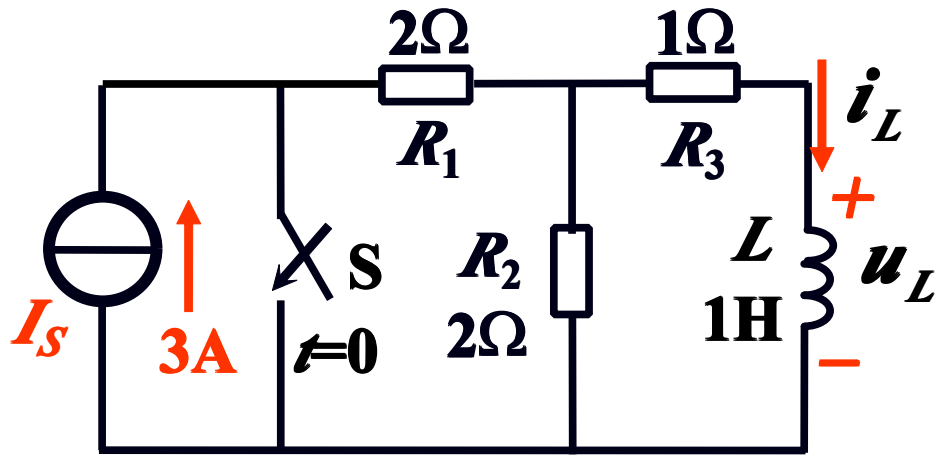

$$i_L(0_+) = i_L(0_-) = 2 \text{ A}$$


$$t = 0_+$$

$$u_L(0_+) = -i_L(0_+) \times \left(\frac{2 \times 2}{2 + 2} + 1 \right) = -4 \text{ V}$$


$$(2) \quad i_L(\infty) \quad u_L(\infty)$$

$$t = \infty$$
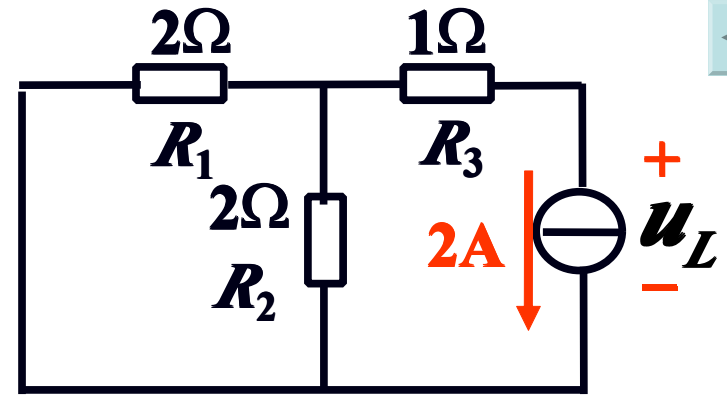
$$i_L(\infty) = 0 \text{ V} \quad u_L(\infty) = 0 \text{ V}$$



$$t = 0_+$$

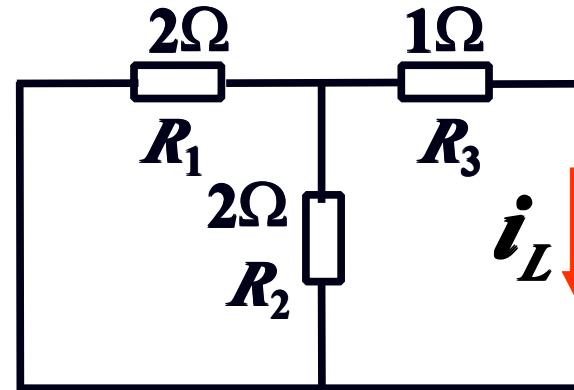

$$t = \infty$$



(3)

$$R_0 = R_1 // R_2 + R_3$$
$$\tau = \frac{L}{R_0} = \frac{1}{2} = 0.5 \text{ s}$$
$$i_L = 0 + (2 - 0) e^{-2t}$$
$$= 2 e^{-2t} \text{ A}$$
$$u_L = 0 + (-4 - 0) e^{-2t}$$
$$= -4 e^{-2t} \text{ V}$$

